

Filling the Blanks

Fill the blanks with most suitable word.

In an electric bulb, the part which does not conduct electricity is the _____
_____.

When a circuit is _____, electricity can flow through.

Wood, rubber, plastic and paper are called _____.

Batteries connected in _____ will result in a higher voltage.

The rubber material that covers bare wires is used as an _____.

Write True or False

1. Electricity is a form of energy. ()
2. When heat flows through a circuit, the heating element of an oven becomes hot. ()
3. When a bulb fuses, it can be reused again after sometime. ()
4. We should connect the positive pole of a battery to the positive pole of another battery. ()
5. A fuse is used to break a circuit when too much electricity flows through. ()